



# RUTGERS

School of Engineering  
Department of Electrical and Computer Engineering

332:494:01/599:02 – Smart Grid – spring 20121  
Homework Assignment – Set 1

**General guidelines for homework assignments:** Homework should be submitted online (via Canvas under the ‘assignment’ Homework 1)

### Question 1:

For the **single-phase** system in Figure 1, it is given that the load  $Z_{Load}$  is consuming  $16kVA$  at a  $pf = 0.6$  *leading*. The voltage across the load  $V_{Load} = 120\angle 0^\circ V(rms)$ . The line impedance is  $Z_{Line} = 1 + j2\Omega$

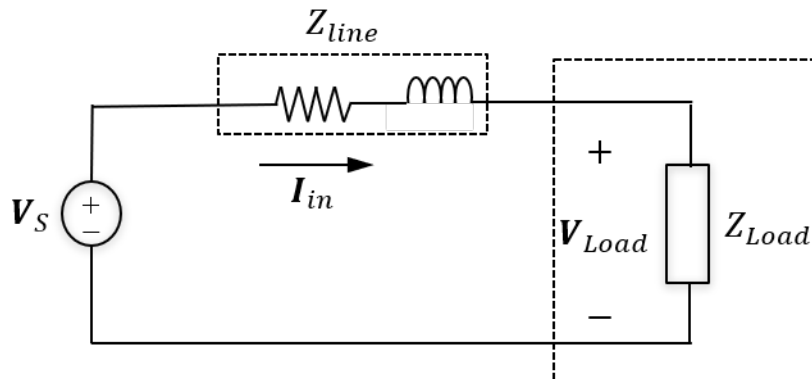


Figure 1

- For the load impedance,  $Z_{Load}$ , draw the power triangle and find (**include units** for each of the first three values):  $P_{Load}$ ;  $Q_{Load}$ ;  $|S_{Load}|$ ;  $S_{Load}$  and the power factor angle  $\theta_{pf}$
- Find the load impedance:  $Z_{load}$
- Find the power losses on the line impedance  $S_{line}(Z_{line})$

### Question 2:

Given the single-phase system in Figure 2, given that:

- $V_{Load} = 13,800\angle 0^\circ V_{rms}$
- Load 1: 60kW at 0.8 power factor **lead**;
- Load 2: 160 kVA at 0.5 power factor **lag**;

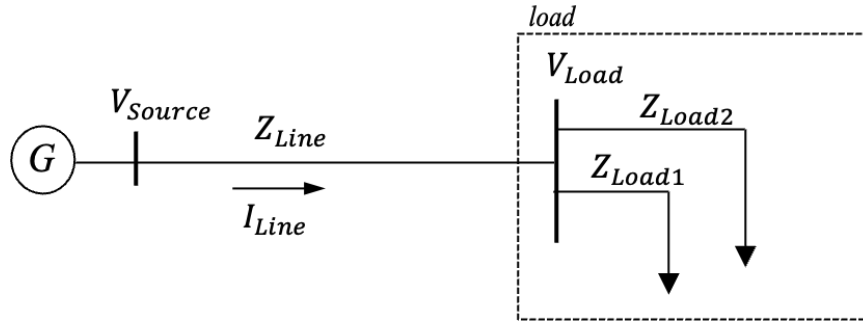


Figure 2

- Find and draw the power triangle for load  $Z_{Load1}$ : what is the real power  $P_{Load1}$  and reactive power  $Q_{Load1}$  consumed by load  $Z_{Load1}$
- Find and draw the power triangle for load  $Z_{Load2}$ : what is the real power  $P_{Load2}$  and reactive power  $Q_{Load2}$  consumed by load  $Z_{Load2}$
- Find the power factor ( $pf$ ) for the total load  $Z_{Load_{eq}} = Z_{Load1} || Z_{Load2}$  and the total apparent power  $|S_{Load_{eq}}|$  in Figure 3

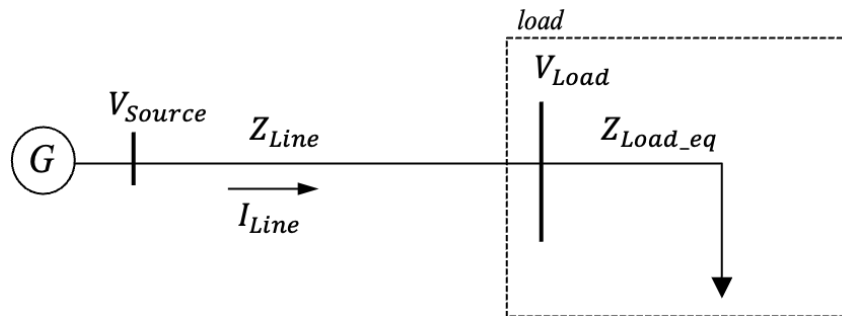


Figure 3

- Find the line current phasor  $I_{line}$
- A capacitor is added in parallel to  $Z_{Load_{eq}}$  (see figure 4). If the power grid frequency is  $f=60\text{Hz}$ , calculate the size of the capacitor  $C_{comp}$  required in order to correct the power factor for the load to 0.95 lag


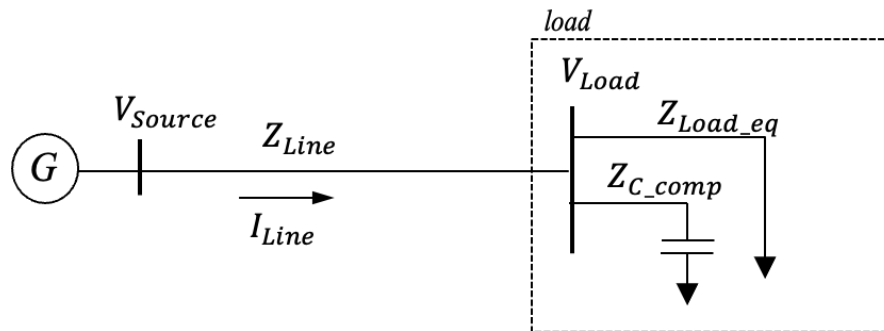


Figure 4

### Question 3:

A small manufacturing plant is located 3km down a transmission line, which has a series reactance of  $j0.4 \Omega/\text{km}$ . The line resistance is negligible. The plant is a three-phase load with a line voltage of 690V (Assume a positive sequence and a phase voltage  $V_{an}$  that serves as reference with angle  $\angle 0^\circ$ ). It consumes 200 kW at 0.85 power factor lagging.

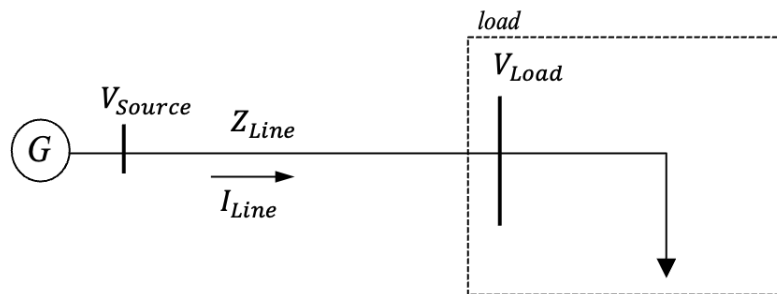- (a) Determine the line voltage at the source
- (b) Determine the 3-phase complex power generated by the source



### Question4:

The following three-phase loads are connected in parallel across a 3,800 V (line-line; Assume a positive sequence and a phase voltage  $V_{an}$  that serves as reference with angle  $\angle 0^\circ$ ) balanced three-phase power network:

Load 1: 120 kVA at 0.9 power factor lag;

Load 2: 180 kW at 0.55 power factor lead;

Load 3: 30 kW at unity power factor.

- (a) Find the total complex power of the three loads
- (b) Find the overall power factor
- (c) Find line current in the supply line