



School of Engineering  
Department of Electrical and Computer Engineering

---

**332:494:01/599:02 – Smart Grid – spring 2021**  
**Homework Assignment – Set 2 SOLUTION**

## Question 1


A balanced Y-connected voltage source with a phase voltage  $V_{an} = 277\angle 0^\circ V$  delivers to a balanced delta connected load with impedance  $Z_{\Delta} = 45 - j18\Omega$  that is in parallel with a Y-connected load with impedance  $Z_Y = 30 + j15\Omega$ .

1. Calculate the total current deliver to the loads

$$\text{Load 1: } Z_{L1} = \frac{Z_{\Delta}}{3} = (15 - j6)\Omega$$

$$\text{Load 2: } Z_{L2} = Z_Y = (30 + j15)\Omega$$
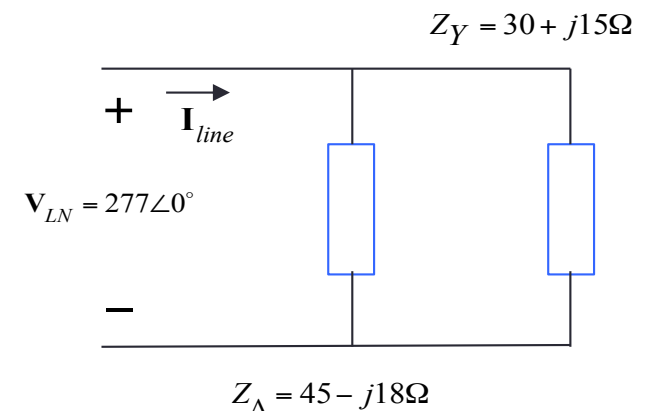
$$I_{Line} = \frac{V_{load.an}}{Z_{L1} \parallel Z_{L2}} = \frac{277\angle 0^\circ}{(15 - j6) \parallel (30 + j15)} = 23.459\angle 6.546^\circ A$$



2. Calculate the total real and reactive power for the loads

$$S_{gen.1\phi} = V_{load.an} \cdot I_{Line}^* = 277\angle 0^\circ \cdot 23.459\angle -6.546^\circ \text{ delivered}$$

$$S_{gen.1\phi} = 6.498\angle -6.546^\circ \text{ kVA delivered}$$

$$S_{gen.3\phi} = 3S_{gen.1\phi} = 19.494\angle -6.546^\circ \text{ kVA delivered}$$

$$P_{gen.3\phi} = 19494 \cdot \cos(-6.546^\circ) = 19.367 \text{ kW delivered}$$


$$Q_{gen.3\phi} = 19494 \cdot \sin(-6.546^\circ) = -2.22 \text{ kVAr delivered}$$

## Question 2

Consider the three-phase system in Figure 1.

From the generator bus (marked as B1) power is delivered to a load of  $150\text{MW}$  and  $60\text{Mvar}$  at bus 3 and a load of  $120\text{MW}$  and  $60\text{MVar}$  at bus 4 (all values in 3-Phase).

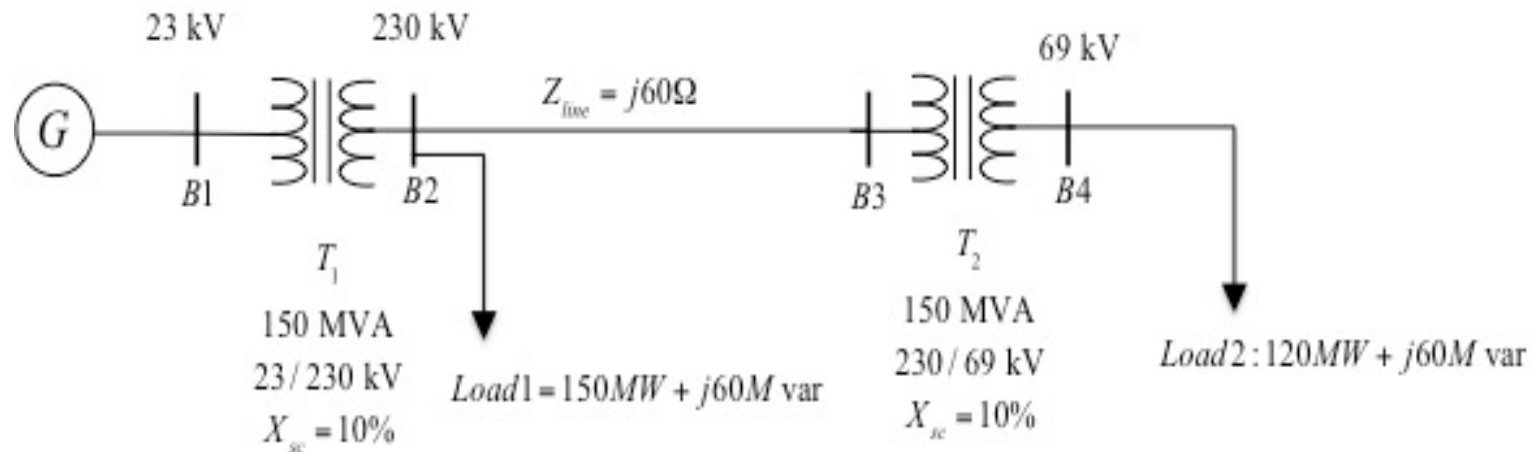The line voltage magnitude at bus 4 (B4) for load 2 needs is kept at  $69\text{ kV}$ .




## Question 2

(a) Find the per-unit representation of the system with a power base value of:



- **Option one:** single-phase value of  $100\text{MVA}$  for the power and phase voltage base value of  $23/\sqrt{3}\text{ kV}$  at bus B1
- **Option two:** three-phase value of  $300\text{MVA}$  for the power and line voltage base value of  $23\text{ kV}$  at bus B1

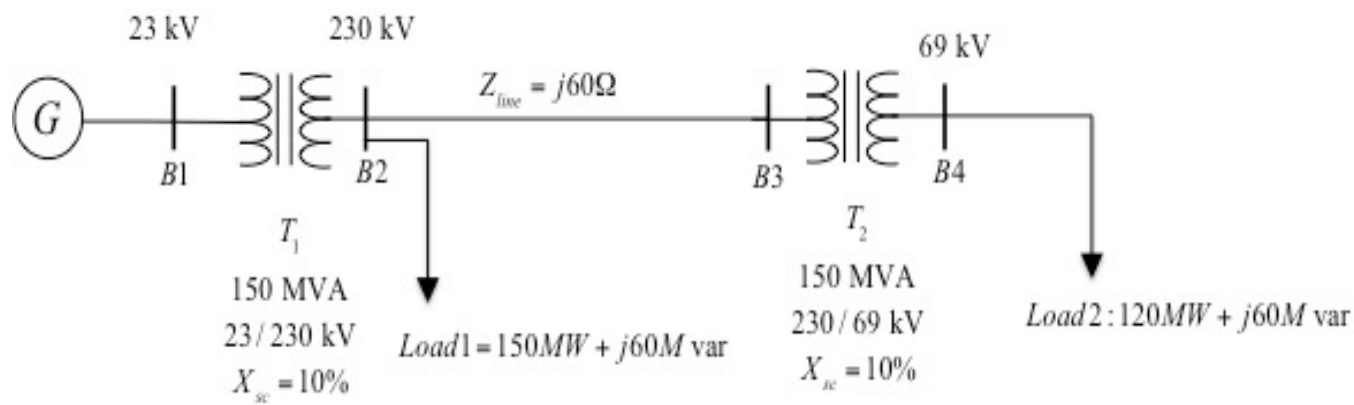**Per the option you chose:**

- Find the base values for the systems in figure 1
- Find all per-unit line impedances: transformers T1 and T2 impedances
- Find all per-unit values for all given powers, impedances, and voltages



## Question 2

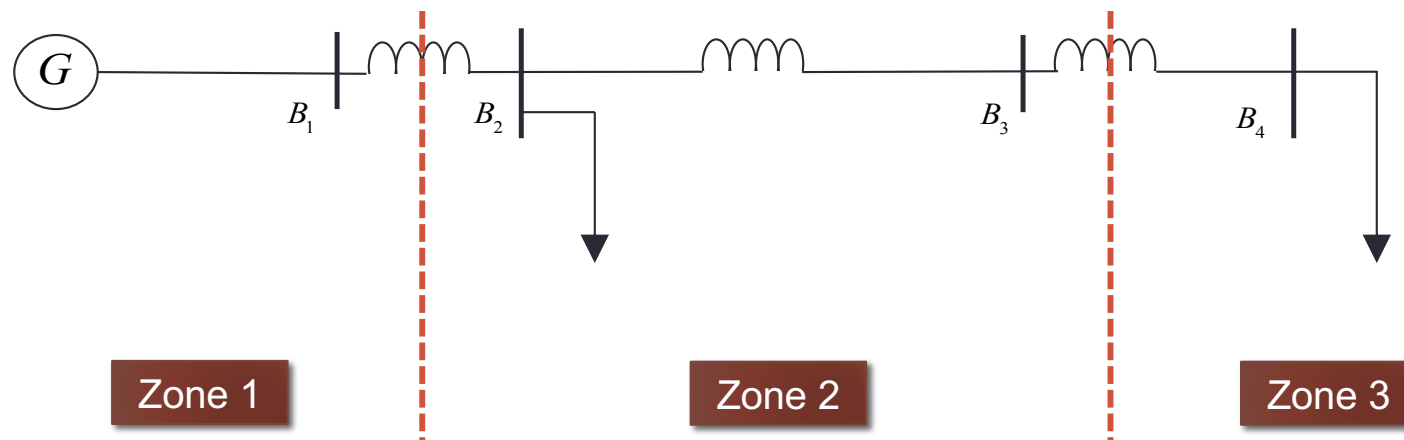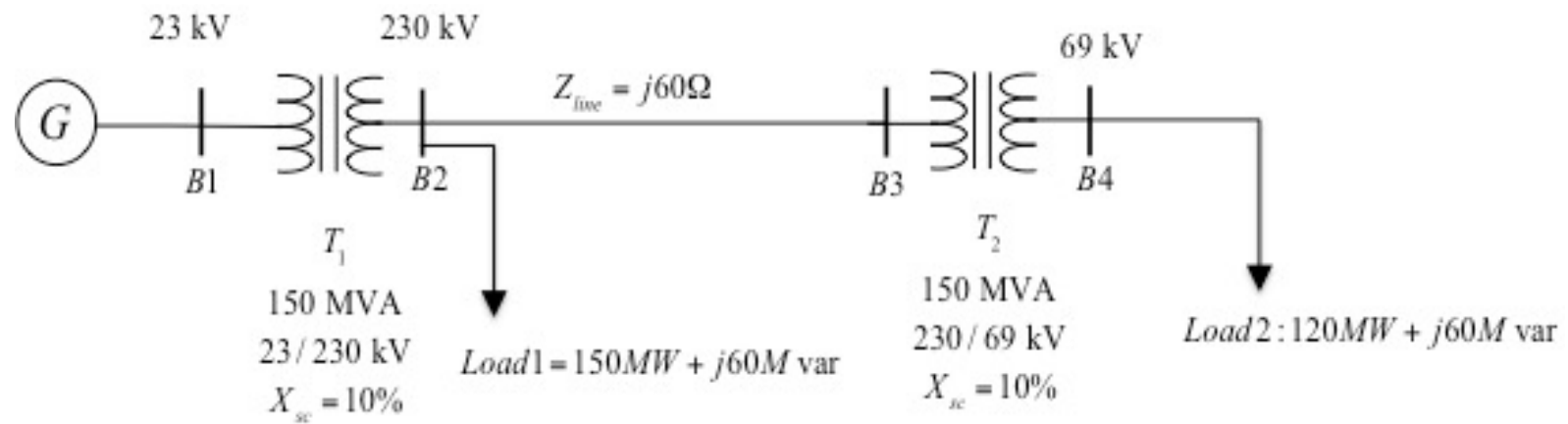

## Question 2

(a) Find the per-unit representation of the system with a power base value of:

**Per the option you chose ... single-phase**

- Find the base values for the systems in figure 1

$S_{b.1\phi} = 100MVA; P_{b.1\phi} = 100MW; Q_{b.1\phi} = 100MVar;$	$I_{b1} = \frac{S_{b.1\phi}}{V_{b1.LN}} = 7.53kA$ $I_{b2} = \frac{S_{b.1\phi}}{V_{2.LN}} = 0.753kA$ $I_{b3} = \frac{S_{b.1\phi}}{V_{3.LN}} = 2.51kA$
$V_{b1.LN} = \frac{23}{\sqrt{3}}kV \rightarrow V_{b2.LN} = V_{b1.LN} \frac{V_{T1.ZN2}}{V_{T1.ZN1}} = \frac{230}{\sqrt{3}}kV$ $V_{b2..LN} = \frac{230}{\sqrt{3}}kV \rightarrow V_{b3.LN} = V_{b2.LN} \frac{V_{T2.ZN3}}{V_{T2.ZN2}} = \frac{69}{\sqrt{3}}kV$	$Z_{b1} = \frac{V_{b1.LN}^2}{S_{b.1\phi}} = 1.7634\Omega$ $Z_{b2} = \frac{V_{b2.LN}^2}{S_{b.1\phi}} = 176.34\Omega$ $Z_{b3} = \frac{V_{b3.LN}^2}{S_{b.1\phi}} = 15.89\Omega$



## Question 2

(a) Find the per-unit representation of the system with a power base value of:

**Per the option you chose ... THREE-phase**


- Find the base values for the systems in figure 1

$S_{b.3\phi} = 300MVA; P_{b.3\phi} = 300MW; Q_{b.3\phi} = 300MVAR;$	$I_{b1} = \frac{S_{b.3\phi}}{\sqrt{3} \cdot V_{b1.LL}} = 7.53kA$
$V_{b1.LL} = 23kV \rightarrow V_{b2.LL} = V_{b1.LL} \frac{V_{T1.ZN2}}{V_{T1.ZN1}} = 230kV$ $V_{b2.LL} = 230kV \rightarrow V_{b3.LL} = V_{b2.LL} \frac{V_{T2.ZN3}}{V_{T2.ZN2}} = 69kV$	$I_{b2} = \frac{S_{b.3\phi}}{\sqrt{3} \cdot V_{2.LL}} = 0.753kA$ $I_{b3} = \frac{S_{b.3\phi}}{\sqrt{3} \cdot V_{3.LL}} = 2.51kA$
	$Z_{b1} = \frac{V_{b1.LL}^2}{S_{b.3\phi}} = 1.7634\Omega$ $Z_{b2} = \frac{V_{b2.LL}^2}{S_{b.3\phi}} = 176.34\Omega$ $Z_{b3} = \frac{V_{b3.LL}^2}{S_{b.3\phi}} = 15.89\Omega$


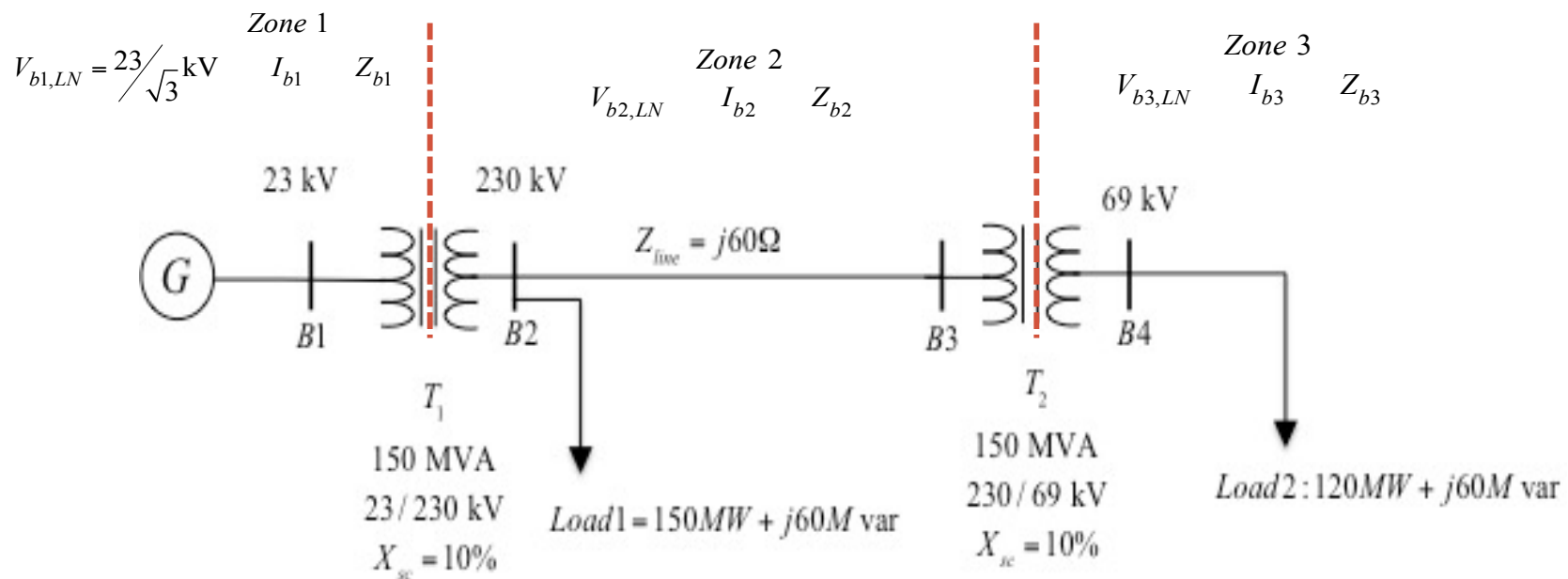
## Question 2


(a.1) Find the base values for the systems in figure 1: with a power base value of 100MVA per-phase (single-phase) and phase voltage base value of  $23/\sqrt{3}$  kV.




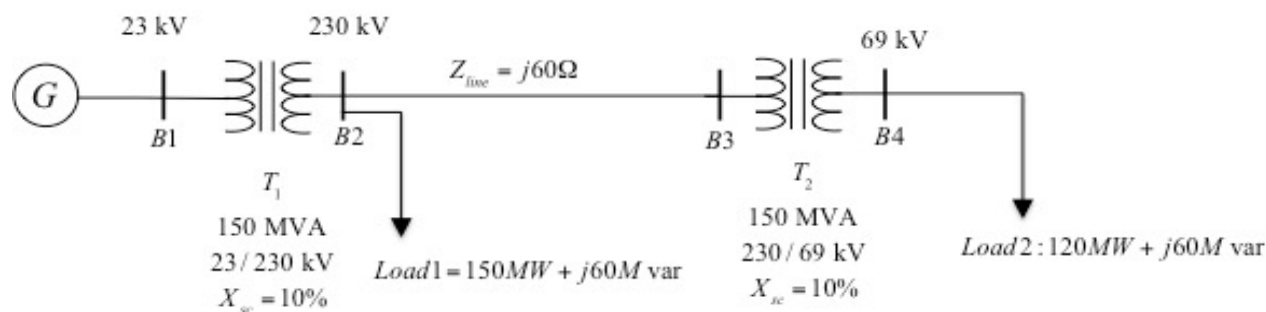
## Question 2

(a.2) Find all per-unit line impedances: transformers T1 and T2 impedances



Single phase base: 
$$Z_{T1} = jX_{T1.sc} \frac{V_{T1.ZN1.LN}^2}{S_{T1.1\phi}} \frac{S_{b.1\phi}}{V_{b1.LN}^2} = j0.1 \frac{(23/\sqrt{3} \cdot 10^3)^2}{150/3 \cdot 10^6} \cdot \frac{100 \cdot 10^6}{(23/\sqrt{3} \cdot 10^3)^2} = j0.2 \text{ pu}$$

$$Z_{T2} = jX_{T2.sc} \frac{V_{T2.ZN2.LN}^2}{S_{T2.1\phi}} \frac{S_{b.1\phi}}{V_{b2.LN}^2} = j0.1 \frac{(230/\sqrt{3} \cdot 10^3)^2}{150/3 \cdot 10^6} \cdot \frac{100 \cdot 10^6}{(230/\sqrt{3} \cdot 10^3)^2} = j0.2 \text{ pu}$$


Three phase base: 
$$Z_{T1} = jX_{T1.sc} \frac{V_{T1.ZN1.LL}^2}{S_{T1.3\phi}} \frac{S_{b.3\phi}}{V_{b1.LL}^2} = j0.1 \frac{(23 \cdot 10^3)^2}{150 \cdot 10^6} \cdot \frac{300 \cdot 10^6}{(23 \cdot 10^3)^2} = j0.2 \text{ pu}$$

$$Z_{T2} = jX_{T2.sc} \frac{V_{T2.ZN2.LL}^2}{S_{T2.3\phi}} \frac{S_{b.3\phi}}{V_{b2.LL}^2} = j0.1 \frac{(230 \cdot 10^3)^2}{150 \cdot 10^6} \cdot \frac{300 \cdot 10^6}{(230 \cdot 10^3)^2} = j0.2 \text{ pu}$$


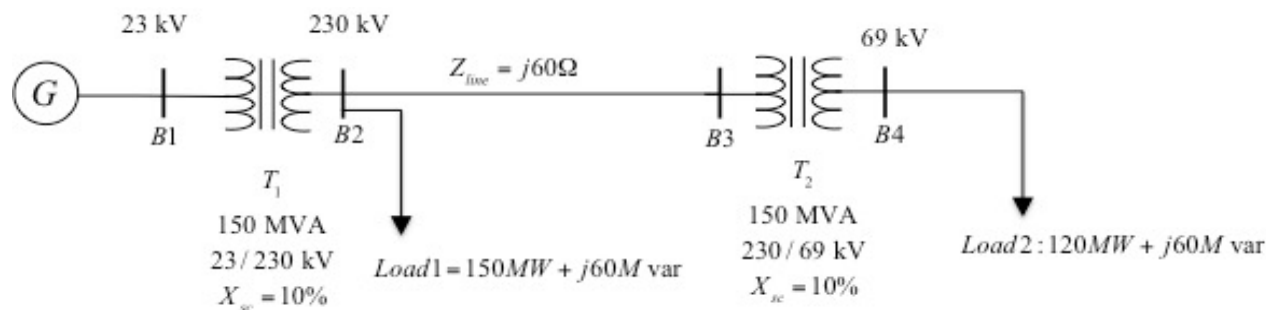
## Question 2

(a.3) Find all per-unit values for all given **powers**, impedances, and voltages



Single phase base:

$$S_{Load1.pu} = \frac{S_{Load1.1\phi}}{S_{b.1\phi}} = \frac{(150 + j60) \cdot 10^6 / 3}{100 \cdot 10^3} = 0.5 + j0.2 \text{ pu}$$

$$S_{Load2.pu} = \frac{S_{Load2.1\phi}}{S_{b.1\phi}} = \frac{(120 + j60) \cdot 10^6 / 3}{100 \cdot 10^3} = 0.4 + j0.2 \text{ pu}$$


Three phase base:

$$S_{Load1.pu} = \frac{S_{Load1.3\phi}}{S_{b.3\phi}} = \frac{(150 + j60) \cdot 10^6}{300 \cdot 10^3} = 0.5 + j0.2 \text{ pu}$$

$$S_{Load2.pu} = \frac{S_{Load2.3\phi}}{S_{b.3\phi}} = \frac{(120 + j60) \cdot 10^6}{300 \cdot 10^3} = 0.4 + j0.2 \text{ pu}$$
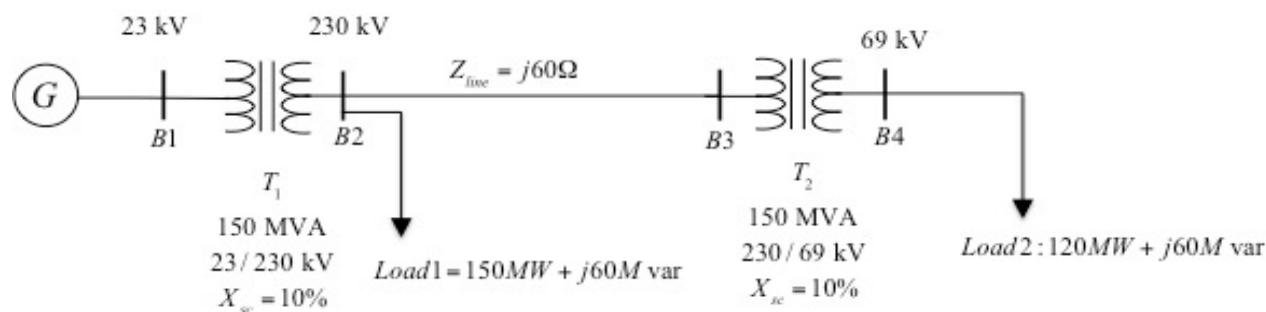
## Question 2

(a.3) Find all per-unit values for all given powers, **impedances, and voltages.**



Single phase base:

$$Z_{Line.pu} = \frac{Z_{line}}{Z_{b2}} = \frac{j60}{176.34} = j0.34 \text{ pu}$$

$$V_{B4.pu} = \frac{V_{B4.LN}}{V_{b3.LN}} = \frac{69/\sqrt{3} \cdot 10^3 \angle 0^\circ}{69/\sqrt{3} \cdot 10^3} = 1 \angle 0^\circ \text{ pu}$$


Three phase base:

$$Z_{Line.pu} = \frac{Z_{line}}{Z_{b2}} = \frac{j60}{176.34} = j0.34 \text{ pu}$$

$$V_{B4.pu} = \frac{V_{B4.LL}}{V_{b3.LL}} = \frac{69 \cdot 10^3 \angle 0^\circ}{69 \cdot 10^3} = 1 \angle 0^\circ \text{ pu}$$


## Question 2

### PU one line diagram:

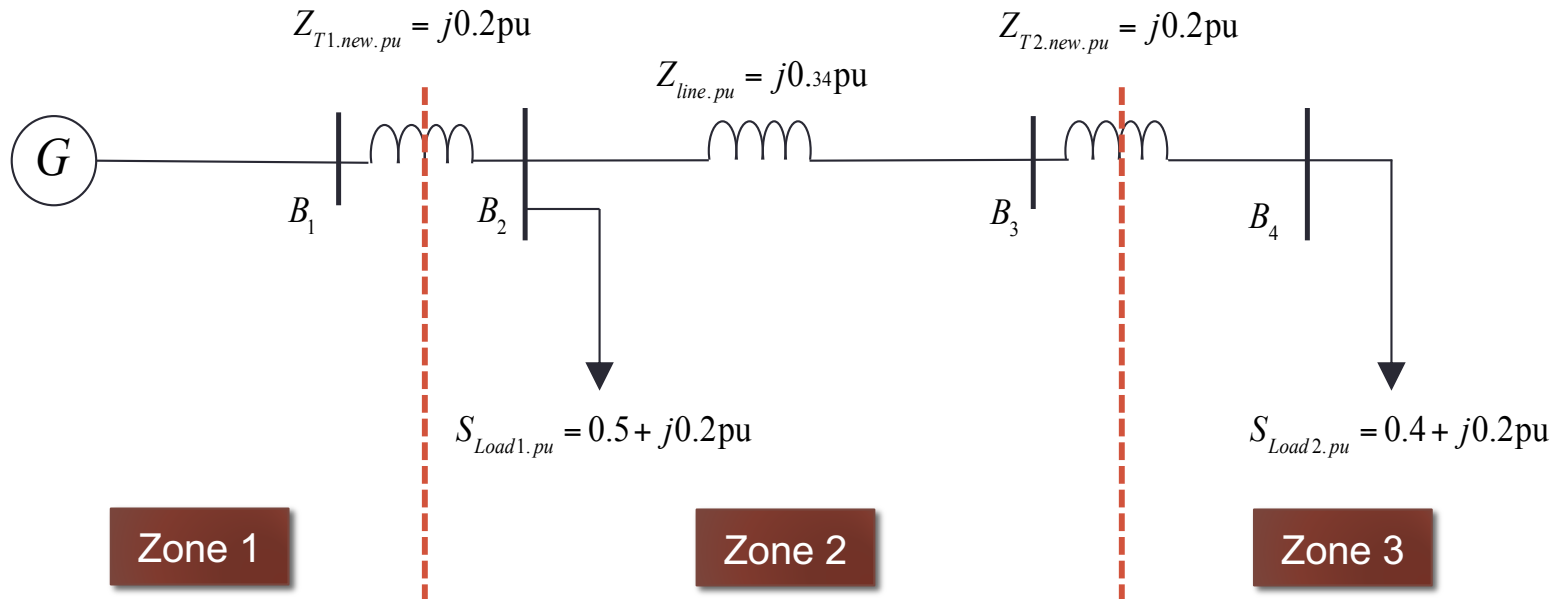

## Question 2

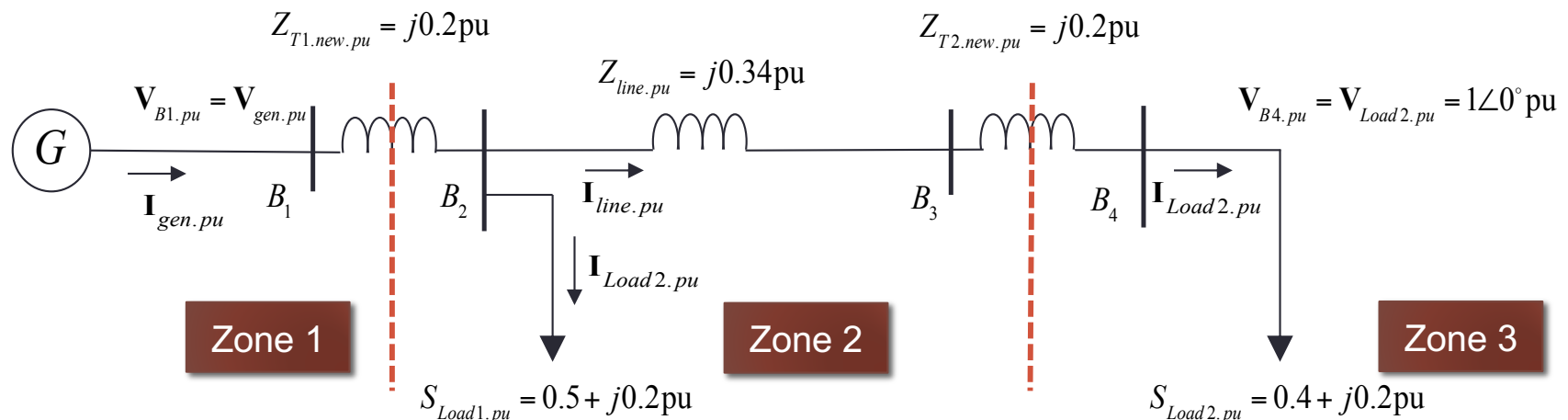(b) What is the line voltage magnitude at the generating source at bus 1 (magnitude of the line voltage at B1)?




The voltage at bus 1 can be calculated as:

$$I_{Line.pu} = I_{Load2.pu} = \frac{S_{load2.pu}^*}{V_{B4.pu}^*} = \frac{0.4 - j0.2}{1 \angle 0^\circ} = 0.4 - j0.2 = 0.4472 \angle -26.565^\circ$$

$$V_{B2.pu} = V_{B1.pu} + I_{Line.pu} (Z_{Line.pu} + Z_{T2.pu})$$

$$V_{B2.pu} = 1 \angle 0^\circ + 0.4472 \angle -26.565^\circ \cdot (j0.34 + j0.2) = 1.108 + j0.216 = 1.129 \angle 11.031^\circ$$

## Question 2

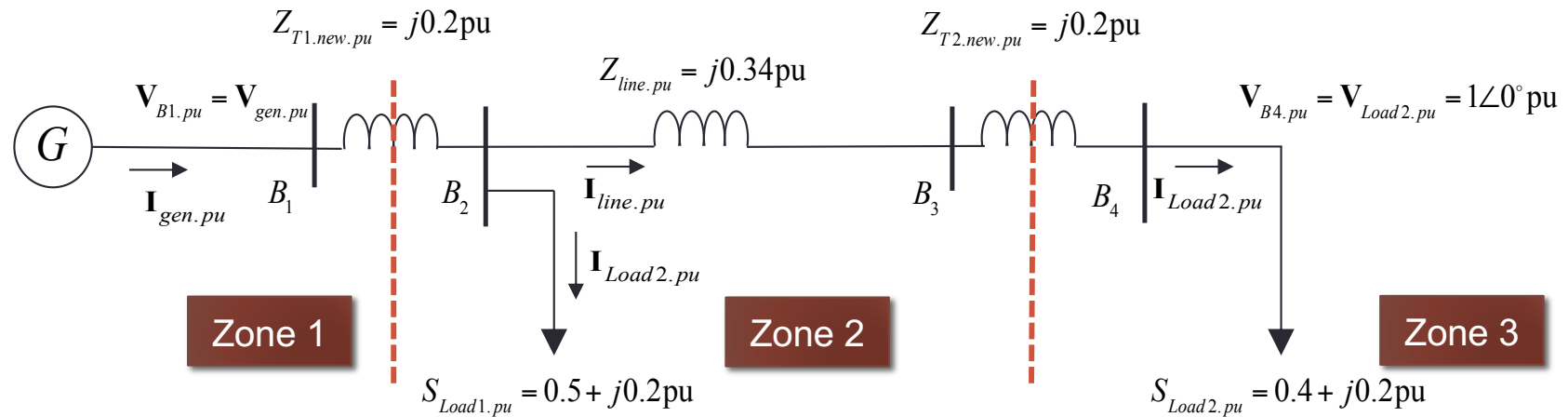

$$V_{B2.pu} = 1\angle 0^\circ + 0.4472\angle -26.565^\circ \cdot (j0.34 + j0.2) = 1.108 + j0.216 = 1.129\angle 11.031^\circ pu$$

$$I_{Load1.pu} = \frac{S_{load1.pu}^*}{V_{B2.pu}^*} = \frac{0.5 - j0.2}{1.129\angle -11.031^\circ} = 0.4686 - j0.089 = 0.477\angle -10.77^\circ pu$$

$$V_{B1.pu} = V_{B2.pu} + I_{gen.pu}(Z_{T1.pu})$$


$$I_{gen.pu} = I_{Load1.pu} + I_{Line.pu} = 0.4686 - j0.089 + 0.4 - j0.2 = 0.8686 - j0.289 = 0.9155\angle -18.41^\circ pu$$

$$V_{B1.pu} = 1.129\angle 11.031^\circ + 0.9155\angle -18.41^\circ \cdot (j0.2) = 1.166 + j0.3897 = 1.229\angle 18.4844^\circ$$

$$|V_{gen.LL}| = |V_{B1.LL}| = |V_{B1.pu}| \cdot V_{b1.LL} = 1.229 \cdot 23k = 28.267kV$$

## Question 2

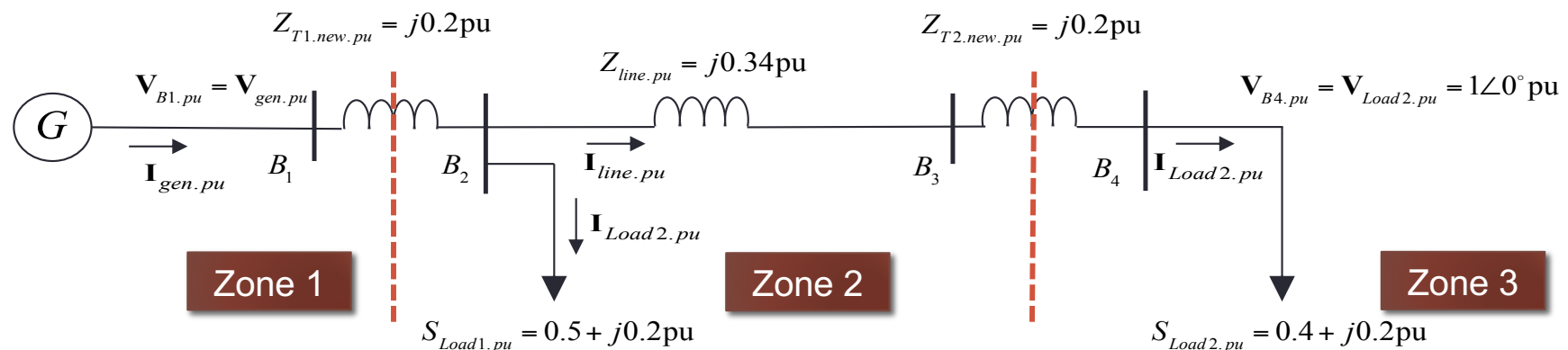(c) Find the real and reactive power for the generator (remember, it's a three-phase system).



The generated power at bus 1 can be calculated as:

$$S_{gen.pu} = V_{gen.pu} I_{gen.pu}^* = V_{B1.pu} I_{gen.pu}^* = 1.229 \angle 18.4844^\circ \cdot (0.9155 \angle 18.41^\circ) = 1.125 \angle 36.89^\circ$$

$$S_{gen} = S_{gen.pu} \cdot S_{b1.3\phi} = 1.125 \angle 36.89^\circ \cdot 300M = 337.5 \angle 36.89^\circ MVA = 270MW + j202.55MVar$$


$$P_{gen} = 270MW$$

$$Q_{gen} = 202.55MVar$$

## Question 3



The three-phase power and line-line voltage ratings are given for the electric power system in figure 2. For the per-unit analysis, a base value of 100MVA is chosen for the three-phase power and a base value of 20kV is chosen for the line voltage on generator 1 end.

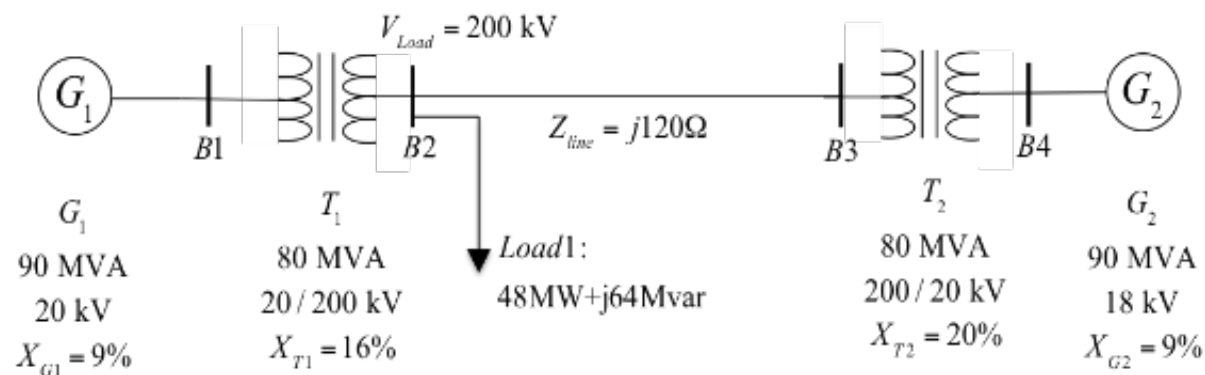- (a) Find the base values for the systems in figure 2
- (a) Find all per-unit line impedances: transformers T1 and T2 impedances; generators G1 and G2 impedances;
- (b) Find all per-unit values for all given powers, and voltages
- (c) Find load1 impedance
- (d) Find the current flow through the load





## Question 3

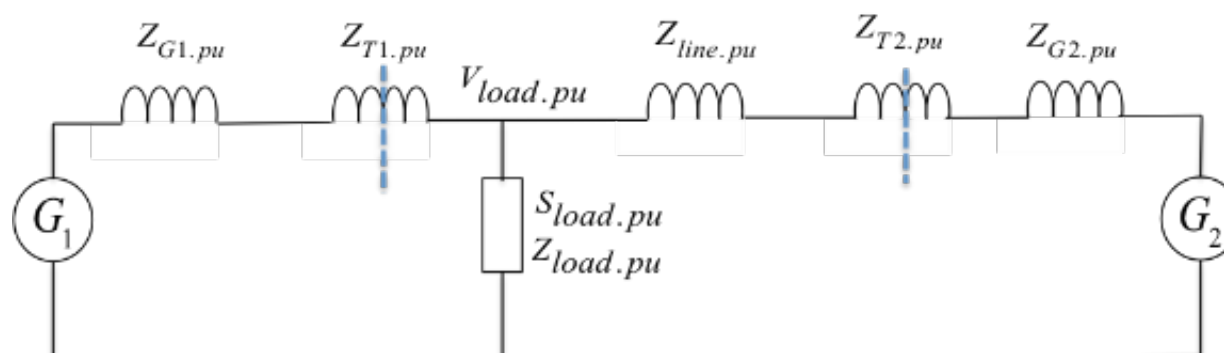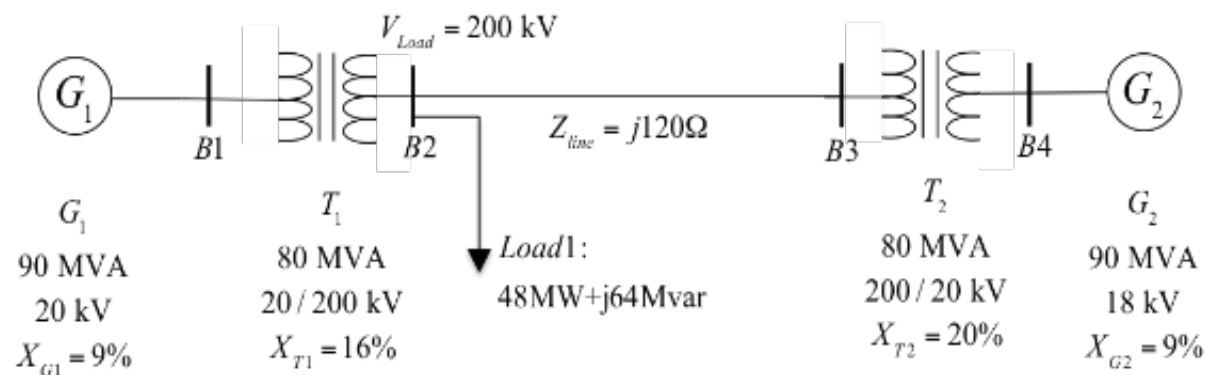

## Question 3

- (a) Find the per-unit representation: **Per the option you chose ... THREE-phase**
- Find the base values for the systems in figure 1

$$S_{b.3\phi} = 100\text{MVA}; P_{b.3\phi} = 100\text{MW}; Q_{b.3\phi} = 100\text{MVar};$$

$$V_{b1.LL} = 20\text{kV}$$


$$V_{b1.LL} = 20\text{kV} \rightarrow V_{b2.LL} = V_{b1.LL} \frac{V_{T1.ZN2}}{V_{T1.ZN1}} = 200\text{kV}$$

$$V_{b2.LL} = 200\text{kV} \rightarrow V_{b3.LL} = V_{b2.LL} \frac{V_{T2.ZN3}}{V_{T2.ZN2}} = 20\text{kV}$$

$$I_{b1} = \frac{S_{b.3\phi}}{\sqrt{3} \cdot V_{b1.LL}} = 2.886\text{kA}$$

$$I_{b2} = \frac{S_{b.3\phi}}{\sqrt{3} \cdot V_{b2.LL}} = 0.2886\text{kA}$$
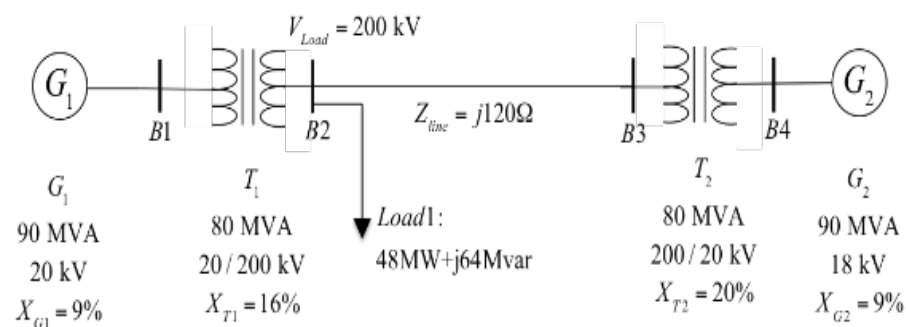
$$I_{b3} = \frac{S_{b.3\phi}}{\sqrt{3} \cdot V_{b3.LL}} = 2.886\text{kA}$$



$$Z_{b1} = \frac{V_{b1.LL}^2}{S_{b.3\phi}} = 4\Omega$$

$$Z_{b2} = \frac{V_{b2.LL}^2}{S_{b.3\phi}} = 400\Omega$$

$$Z_{b3} = \frac{V_{b3.LL}^2}{S_{b.3\phi}} = 4\Omega$$



## Question 3

Part (a):

$S_{b,3\phi} = 100 \text{ MVA}$			
	zone 1	zone 2	zone 3
$V_{bi,LL}$	20 kV	200 kV	20 kV
$I_{bi}$	2.886 kA	0.2886 kA	2.886 kA
$Z_{bi}$	$4\Omega$	$400\Omega$	$4\Omega$

## Question 3

- (a) Find all per-unit line impedances: transformers T1 and T2 impedances; generators G1 and G2 impedances.

$$Z_{T1} = jX_{T1.sc} \frac{V_{T1.ZN1.LL}^2}{S_{T1.3\phi}} \frac{S_{b.3\phi}}{V_{b1.LL}^2} = j0.16 \frac{(20 \cdot 10^3)^2}{80 \cdot 10^6} \cdot \frac{100 \cdot 10^6}{(20 \cdot 10^3)^2} = j0.2 \text{ pu}$$

$$Z_{T2} = jX_{T2.sc} \frac{V_{T2.ZN2.LL}^2}{S_{T2.3\phi}} \frac{S_{b.3\phi}}{V_{b2.LL}^2} = j0.2 \frac{(200 \cdot 10^3)^2}{80 \cdot 10^6} \cdot \frac{100 \cdot 10^6}{(200 \cdot 10^3)^2} = j0.25 \text{ pu}$$

$$Z_{G1} = jX_{G1.sc} \frac{V_{G1.LL}^2}{S_{G1.3\phi}} \frac{S_{b.3\phi}}{V_{b1.LL}^2} = j0.09 \frac{(20 \cdot 10^3)^2}{90 \cdot 10^6} \cdot \frac{100 \cdot 10^6}{(20 \cdot 10^3)^2} = j0.1 \text{ pu}$$

$$Z_{G2} = jX_{G2.sc} \frac{V_{G2.LL}^2}{S_{G2.3\phi}} \frac{S_{b.3\phi}}{V_{b3.LL}^2} = j0.09 \frac{(18 \cdot 10^3)^2}{90 \cdot 10^6} \cdot \frac{100 \cdot 10^6}{(20 \cdot 10^3)^2} = j0.081 \text{ pu}$$

## Question 3

(b) Find all per-unit values for all given powers, and voltages

$$S_{Load1.pu} = \frac{S_{Load1.3\phi}}{S_{b.3\phi}} = \frac{(48 + j64) \cdot 10^6}{100 \cdot 10^6} = 0.48 + j0.64 \text{ pu}$$

$$V_{Load1.pu} = \frac{V_{Load1.LL}}{V_{b2.LL}} = \frac{200 \cdot 10^3}{200 \cdot 10^3} = 1 \angle 0^\circ \text{ pu}$$

$$Z_{Line.pu} = \frac{Z_{Line}}{Z_{b2}} = \frac{j120}{400} = j0.3 \text{ pu}$$

(c) Find load1 impedance:

$$Z_{Load1.pu} = \frac{|V_{Load1.pu}|^2}{S_{Load1.pu}^*} = \frac{1}{0.48 - j0.64} = 1.25 \angle -53.13^\circ \text{ pu}$$

$$Z_{Load1} = Z_{Load1.pu} \cdot Z_{b2} = 1.25 \angle -53.13^\circ \cdot 400 = 300 + j400 \Omega$$

## Question 3

(d) Find the current flow through the load

$$I_{Load1,pu} = \frac{S_{Load1,pu}^*}{V_{Load1,pu}^*} = \frac{0.48 - j0.64}{1 \angle 0^\circ} = 0.48 - j0.64 \text{ pu}$$

$$I_{Load1} = I_{Load1,pu} \cdot I_{b2} = (0.48 - j0.64) \cdot 288.6 = 138.53 - j184.7 \text{ A} = 230.88 \angle -53.13^\circ \text{ A}$$