



RUTGERS

School of Engineering
Department of Electrical and Computer Engineering

332:494:01/599:02 – Smart Grid – spring 2021
Homework Assignment – Set 1

General guidelines for homework assignments: Homework should be submitted online (via Canvas under the ‘assignment’ Homework 1)

Question 1:

For the **single-phase** system in Figure 1, it is given that the load Z_{Load} is consuming $16kVA$ at a $pf = 0.6$ *leading*. The voltage across the load $V_{Load} = 120\angle 0^\circ V(rms)$. The line impedance is $Z_{Line} = 1 + j2\Omega$

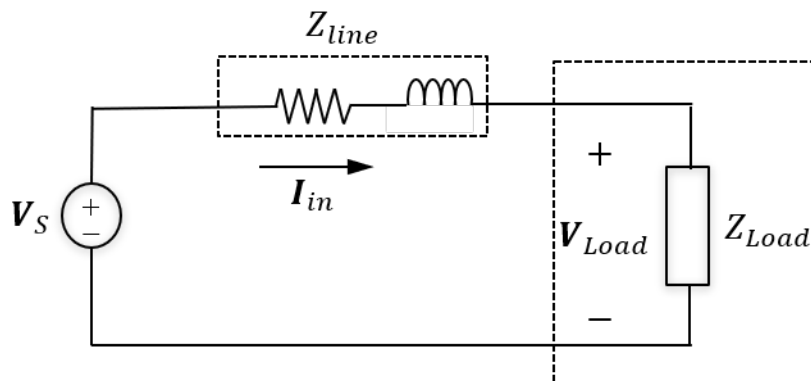


Figure 1

- (a) For the load impedance, Z_{Load} , draw the power triangle and find (**include units** for each of the first three values): P_{Load} ; Q_{Load} ; $|S_{Load}|$; S_{Load} and the power factor angle θ_{pf}

$$\begin{aligned}
 |S_{Load}| &= 16 \text{ kVA} \\
 pf = 0.6 \text{ lead} &\rightarrow \theta_{pf} = -\cos^{-1}(0.6) = -53.13^\circ \\
 \rightarrow P_{Load} &= |S_{Load}| \cdot pf = 9.6 \text{ kW}; \quad P_{Load} = 9.6 \text{ kW} \\
 Q_{Load} &= |S_{Load}| \cdot \sin(-53.13^\circ) = -12.8 \text{ kVAr} \\
 Q_{Load} &= -12.8 \text{ kVAr}
 \end{aligned}$$

$$S_{Load} = 9.6 \text{ kW} - j12.8 \text{ kVAr} = 16 \text{ kVA} \angle -53.13^\circ$$

(b) Find the load impedance: Z_{load}

$$Z_{load} = \frac{|V_{Load}|^2}{S_{Load}^*} = \frac{|120|^2}{16kVA \angle 53.13^\circ} = 0.9 \angle -53.13^\circ \Omega$$

$$Z_{load} = 0.54 - j0.72 \Omega$$

(c) Find the power losses on the line impedance $S_{line}(Z_{line})$

$$Z_{Line} = 1 + j2 \Omega$$

$$I_{Line} = I_{Load} = \frac{S_{Load}^*}{V_{Load}^*} = \frac{16kVA \angle 53.13^\circ}{120 \angle 0^\circ} = 133.34 \angle -53.13^\circ A$$

$$S_{line} = |I_{Line}|^2 \cdot Z_{Line} = (133.34)^2 (1 + j2) = 17.778kW + j35.556kVAr$$

Question 2:

Given the single-phase system in Figure 2, given that:

- $V_{Load} = 13,800 \angle 0^\circ V_{rms}$
- Load 1: 60kW at 0.8 power factor **lead**;
- Load 2: 160 kVA at 0.5 power factor **lag**;

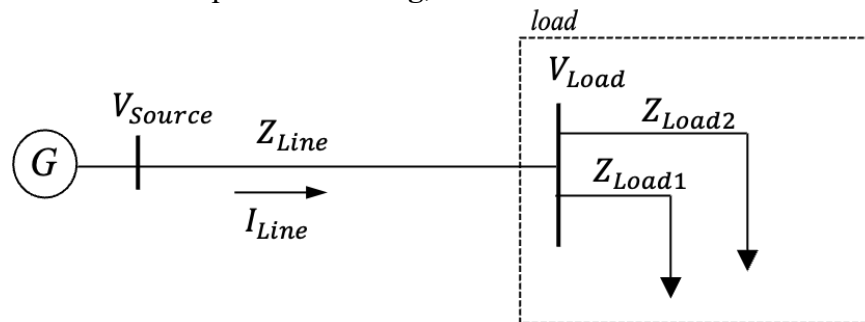


Figure 2

(a) Find and draw the power triangle for load Z_{Load1} : what is the real power P_{Z1} and reactive power Q_{Z1} consumed by load Z_{Load1}

$$P_{Z1} = 60 \text{ kW}; \theta_{pf1} = -\cos^{-1}(0.8) = -36.87^\circ$$

$$\rightarrow |S_{Z1}| = \frac{P_{Z1}}{pf1} = 75 \text{ kVA}; |S_{Z1}| = 75 \text{ kVA}$$

$$Q_{Z1} = P_{Z1} \cdot \tan(-36.87^\circ) = |S_{Z1}| \cdot \sin(-36.87^\circ) = -45 \text{ kVAr}$$

$$Q_{Z1} = -45 \text{ kVAr}$$

- (b) Find and draw the power triangle for load Z_{Load2} : what is the real power P_{Z2} and reactive power Q_{Z2} consumed by load Z_{Load2}

$$|S_{Z2}| = 160 \text{ kVA}; \theta_{pf2} = \cos^{-1}(0.5) = 60^\circ$$

$$\rightarrow P_{Z2} = |S_{Z2}| \cdot \cos(60^\circ) = 80 \text{ kW}; \text{ } P_{Z2} = 80 \text{ kW}$$

$$Q_{Z2} = |S_{Z2}| \cdot \sin(60^\circ) = 138.564 \text{ kVAr}$$

$$Q_{Z2} = 138.564 \text{ kVAr}$$

- (c) Find the power factor (pf) for the total load $Z_{Load_eq} = Z_{Load1} || Z_{Load2}$ and the total apparent power $|S_{Load_eq}|$ in Figure 3

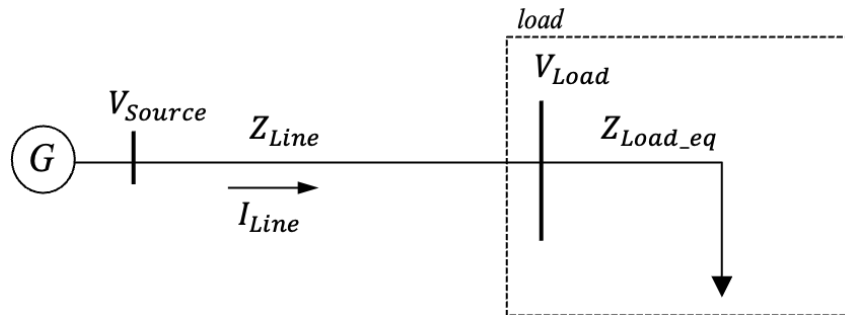


Figure 3

$$\rightarrow P_{Zeq} = P_{Z1} + P_{Z2} = 140 \text{ kW};$$

$$\rightarrow Q_{Zeq} = Q_{Z1} + Q_{Z2} = 93.564 \text{ kVAr}$$

$$\rightarrow |S_{Zeq}| = \sqrt{P_{Zeq}^2 + Q_{Zeq}^2} = 168.387 \text{ kVA}$$

$$|S_{Z2}| = 168.387 \text{ kVA}$$

$$\theta_{pf(eq)} = \tan^{-1}\left(\frac{Q_{Zeq}}{P_{Zeq}}\right) = 33.755^\circ$$

$$pf_{eq} = \cos(33.755^\circ) = 0.83$$

$$pf_{eq} = 0.83$$

- (d) Find the line current phasor I_{line}

$$I_{Line} = I_{Load} = \frac{S_{Zeq}^*}{V_{Load}^*} = \frac{168.387 \cdot 10^3 \angle -33.755^\circ}{13,800 \angle 0^\circ} = 12.2 \angle -33.755^\circ \text{ A}$$

- (e) A capacitor is added in parallel to Z_{Load_eq} (see figure 4). If the power grid frequency is $f=60\text{Hz}$, calculate the size of the capacitor C_{comp} required in order to correct the power factor for the load to 0.95 lag

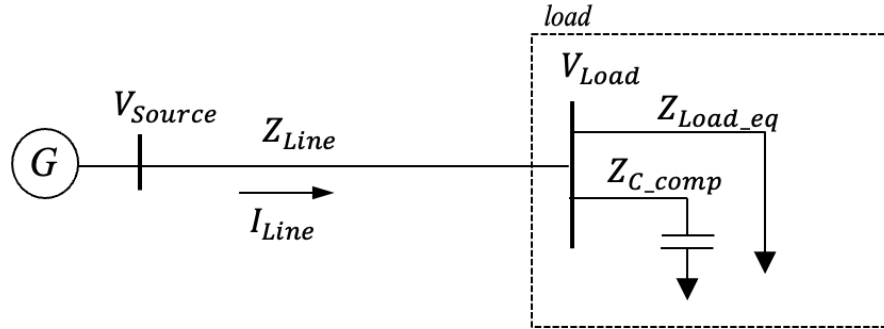


Figure 4

$$\theta_{pf(new)} = \cos^{-1}(0.95) = 18.195^\circ$$

$$\frac{Q_{Znew}}{P_{Zeq}} = \tan(\theta_{pf(new)}) = 0.3287 \rightarrow Q_{Znew} = 0.3287 \cdot 140kW = 46.016kVar$$

$$Q_{CAP} + Q_{Zeq} = Q_{Znew}$$

$$\rightarrow Q_{CAP} = Q_{Znew} - Q_{Zeq} = 46.016k - 93.564k = -47.548kVar$$

$$S_{cap} = jQ_{CAP} = -j47.548kVar$$

$$Z_{CAP} = \frac{|V_{Load}|^2}{S_{cap}^*} = \frac{13,800^2}{(-j47.548 \cdot 10^3)^*} = -j4005.216$$

$$Z_{CAP} = -j \frac{1}{\omega \cdot C_{cap}} \rightarrow C_{cap} = \frac{1}{\omega \cdot |Z_{CAP}|} = \frac{1}{2\pi 60 \cdot 4005.216} = 0.6623 \mu F$$

Question 3:

A small manufacturing plant is located 3km down a transmission line, which has a series reactance of $j0.4 \Omega/\text{km}$. The line resistance is negligible. The plant is a three-phase load with a line voltage of 690V (Assume a positive sequence and a phase voltage V_{an} that serves as reference with angle $\angle 0^\circ$). It consumes 200 kW at 0.85 power factor lagging.

(a) Determine the line voltage at the source

$$V_{Load.LN} = \frac{|V_{Load.LL}|}{\sqrt{3}} \angle 0^\circ = \frac{690}{\sqrt{3}} \angle 0^\circ = 398.37 \angle 0^\circ V$$

(LN → line-to-neutral voltage or phase voltage; LL → line-to-line voltage or line voltage)

$$Z_{Line} = d \cdot Z_{Line-per-km} = 3 \cdot j0.4 = j1.2\Omega$$

Given the info for the load:

$$P_{load.3\phi} = 200 kW; \theta_{pfload} = \cos^{-1}(0.85) = 31.788^\circ$$

$$\rightarrow |S_{load.3\phi}| = \frac{P_{load}}{\cos \theta_{pfload}} = 235.29 kVA; |S_{load.3\phi}| = 235.29 kVA$$

$$Q_{load.3\phi} = P_{load.3\phi} \cdot \tan(31.788^\circ) = |S_{load.3\phi}| \cdot \sin(31.788^\circ) \\ = \mathbf{123.95 \text{ kVAr}} \\ \mathbf{Q_{load.3\phi} = 123.95 \text{ kVAr}}$$

$$S_{source.1\phi} = \frac{S_{source.3\phi}}{3} = 66.67 \text{ kW} + j41.3167 \text{ kVAr} = 78.43 \angle 31.788^\circ \text{ kVA}$$

We can use the load power and voltage to calculate the load current (which in this case is the same as the line current):

$$I_{Line} = I_{Load} = \frac{S_{load.1\phi}^*}{V_{Load.LN}^*} = \frac{(78.43 \cdot 10^3 \angle -31.788^\circ)}{398.37 \angle 0^\circ} = 196.879 \angle -31.788^\circ \text{ A}$$

The voltage on the source side can be found using node voltages across the line impedance:

$$\frac{V_{Source.LN} - V_{Load.LN}}{Z_{Line}} = I_{Line}$$

$$\rightarrow V_{Source.LN} = V_{Load.LN} + I_{Line} \cdot Z_{Line} = 398.37 \angle 0^\circ + 196.879 \angle -31.788^\circ \cdot 1.2 \angle 90^\circ \\ V_{Source.LN} = 522.82 + 200.82 = 560.06 \angle 21.012^\circ \text{ V} \\ |V_{Source.LL}| = \sqrt{3} \cdot |V_{Source.LN}| = 970.06 \text{ V}$$

(b) Determine the 3-phase complex power **generated** by the source

$$S_{source.3\phi} = 3 \cdot S_{source.1\phi} = 3 \cdot V_{Source.LN} \cdot I_{source}^* \\ I_{source} = I_{Line} \\ \rightarrow S_{source.3\phi} = 3 \cdot 560.06 \angle 21.012^\circ \cdot 196.879 \angle 31.788^\circ \\ = 330.79 \text{ kVA} \angle 52.8^\circ \text{ generated} \\ S_{source.3\phi} = 200 \text{ kW} + j263.48 \text{ kVAr generated}$$


We can either mark that this real and reactive power is generated or assign the right sign:

$$S_{source.3\phi} = 3 \cdot S_{source.1\phi} = 3 \cdot (-V_{Source.LN} \cdot I_{source}^*)$$

$$S_{source.3\phi} = -200 \text{ kW} - j263.48 \text{ kVAr}$$

Another way to solve would be:

$$S_{source.3\phi} = S_{line.3\phi} + S_{load.3\phi} = 3|I_{Line}|^2 \cdot Z_{Line} + S_{load.3\phi}$$

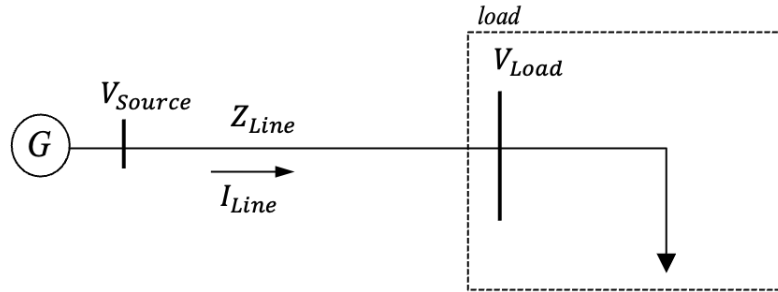

Question4:

The following three-phase loads are connected in parallel across a 3,800 V (line-line; Assume a positive sequence and a phase voltage V_{an} that serves as reference with angle $\angle 0^\circ$) balanced three-phase power network:

Load 1: 120 kVA at 0.9 power factor lag;

Load 2: 180 kW at 0.55 power factor lead;

Load 3: 30 kW at unity power factor.

(a) Find the total complex power of the three loads

Given:

$$S_{L1.3\phi} = 120 \text{ kVA}; pf_{L1} = 0.9 \text{ lag} \Rightarrow \theta_{L1} = 25.84^\circ$$

$$P_{L1.3\phi} = S_{L1.3\phi} \cos(\theta_{L1}) = 108 \text{ kW}; Q_{L1.3\phi} = S_{L1.3\phi} \sin(\theta_{L1}) = 52.3 \text{ kVAr}$$

$$P_{L2.3\phi} = 180 \text{ kW}; pf_{L2} = 0.55 \text{ lead} \Rightarrow \theta_{L2} = -56.63^\circ$$

$$Q_{L2.3\phi} = S_{L2.3\phi} \sin(\theta_{L2}) = \frac{P_{L2.3\phi}}{\cos(\theta_{L2})} \sin(\theta_{L2}) = -273.33 \text{ kVAr}$$

$$P_{L3.3\phi} = 30 \text{ kW}; pf_{L3} = 1 \Rightarrow \theta_{L3} = 0^\circ$$

$$Q_{L3.3\phi} = 0 \text{ kVAr}$$

$$S_{loas.3\phi} = P_{L1.3\phi} + P_{L2.3\phi} + P_{L3.3\phi} + Q_{L1.3\phi} + Q_{L2.3\phi} + Q_{L3.3\phi}$$

$$S_{loas.3\phi} = 318 \text{ kW} - j221.03 \text{ kVAr} = 387.27 \angle -34.8^\circ \text{ kVA}$$

(b) Find the overall power factor

$$pf_{Load} = \cos(\angle -34.8^\circ) = 0.821 \text{ lead}$$

(c) Find line current in the supply line

$$|V_{Load.LL}| = 3,800 \text{ V}$$

$$V_{Load.LN} = \frac{|V_{Load.LL}|}{\sqrt{3}} \angle 0^\circ = \frac{3,800}{\sqrt{3}} \angle 0^\circ = 2193.93 \angle 0^\circ \text{ V}$$

$$S_{Load.1\phi} = \frac{S_{3\phi total}}{3} = 129.09 \cdot 10^3 \angle -34.8^\circ$$

$$\Rightarrow I_{line} = I_{load} = \left(\frac{S_{1\phi total}}{V_{Load.LN}} \right)^* = \left(\frac{129.09 \cdot 10^3 \angle -34.8^\circ}{2193.93 \angle 0^\circ} \right)^* = 58.84 \angle 34.8^\circ \text{ A}$$