



# RUTGERS

School of Engineering  
Department of Electrical and Computer Engineering

## 332:494:01/599:02 – Smart Grid – Spring 2021 Homework Assignment – Set 3

**General guidelines for homework assignments:** Homework should be submitted online (via Canvas)

### Question 1:

A three-phase overhead transmission line is designed to deliver 100 MVA at 220 kV line voltage over a distance of 100 km.


If the  $I^2R$  losses need to be kept to a maximum of 3% of the rated line MVA, given the resistivity of the conductor material to be  $2.84 \times 10^{-8} \Omega \cdot m$ , determine the required conductor diameter (in inches or mils) and the conductor size in circular mils.

Remark: neglect any other line losses (other than resistivity)

### Question 2:

A 230kV three phase transmission line has a per phase series impedance of  $z = 0.05 + j0.45\Omega$  per km and a per phase shunt admittance of  $y = j3.4 \times 10^{-6} \Omega^{-1}$  per km. The line is 80km long. Using the medium line  $\pi$  model:

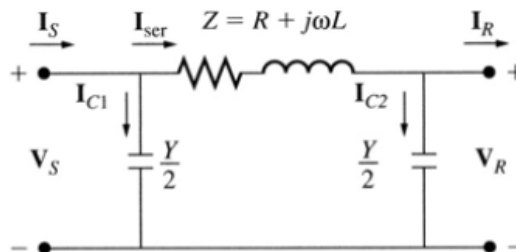(a) Determine the transmission line model:  $Z$  and  $Y/2$



$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

- (b) Determine the constants  $A, B, C$ , and  $D$  for:
- (c) Find the sending end (generating) voltage  $V_s$ , current  $I_s$ , and generated power  $S_{source}$  when the line delivers to a load of:
  1. 200 MVA with 0.8 lagging power factor at 220 kV
  2. 306 MVA with unity power factor at 220 kV

### Question 3:

- a. Given that the external diameter of a cable is 0.84" and the cables are located horizontally such that  $D_{ab} = 10ft$ ,  $D_{bc} = 10ft$  and  $D_{ca} = 20ft$ , what is the shunt capacitor per mile  $Y_C =$  \_\_\_\_\_ [ $\Omega^{-1} \cdot \text{mile}$ ] or [ $\Omega^{-1} \cdot \text{m}$ ]
- b. Given that the GMR of a cable is 0.16ft and the cables are located horizontally such that  $D_{ab} = 10ft$ ,  $D_{bc} = 10ft$  and  $D_{ca} = 20ft$ , what is the line inductive reactance per mile per phase  $X_L =$  \_\_\_\_\_ [ $\Omega / \text{mile}$ ] or [ $\Omega / \text{m}$ ]

Remark: the grid frequency is assumed to be  $f = 60\text{Hz}$ .

### Question 4:

Consider a 3-phase hydropower generator feeding power into the grid bus, which is held at line voltage of 26kV. The internal reactance is 0.8pu for a rated power of 30MVA.

- (a) Choose as base value  $S_{b,3\phi} = 30\text{MVA}$  and  $V_{b,LL} = 26\text{kV}$  and calculate the per-unit values for the power and grid voltage.
- (b) Assume the generator initially runs overexcited with  $|E| = 1.3\text{ pu}$  and a real power output of  $P_e = 0.32\text{ pu}$ . Compute the reactive power and the apparent power output of the generator as measured at the grid bus.
- (c) For the case in (b) find the power factor
- (d) Assume the steam valve is opened to generate a 50% increase in power  $P_e$ , what are the new power angle, the reactive power, and the new power factor?
- (e) What can be done to bring back the power factor to the previous value? Explain.
- (f) Assume that from the original initial state we increase the field current such that the armature voltage amplitude is increased by 15%, what will be the resulting reactive power? What will be the resulting power factor?